

1)

i	(sum of/total) current into a junction equals the (sum of/total) current out conservation of charge	B1 B1	total vector sum of currents is zero
ii	(sum of) e.m.f.s = (sum /total of) p.d.s/sum of voltages in/around a (closed) loop (in a circuit) energy is conserved	B1 B1	

2)

a	current moves from + to – (of battery in circuit) <b>and</b> electrons move from – to +	B1	
b	$C s^{-1} V \Omega^{-1}$	B1 B1	2 correct 2 marks; 1 correct 1 mark, withhold a mark for each additional answer given
c	i statement of Kirchhoff's first law or conservation of charge	B1	<b>accept</b> wires are in <u>series</u> or current is the same (at every point) in a <u>series</u> circuit/AW <b>not</b> current in = current out

3)

a	i	$E = (Pt) = 36 \times 3600 = 1.3 \times 10^5 (J)$	C1 A1	<b>allow</b> $I = 3 A$ and $E = VIt$ , etc. <b>accept</b> 129600 (J)
	ii	$Q = E/V = 1.3 \times 10^5/12$ <b>or</b> $Q = It = 3 \times 3600 = 1.1 \times 10^4$ unit: C	C1 A1 B1	<b>ecf (a)(i)</b> <b>accept</b> $1.08 \times 10^4$ <b>allow</b> $A s$ <b>not</b> $J V^{-1}$
	iii	$Q/e = 1.1 \times 10^4/1.6 \times 10^{-19} = 6.9 \times 10^{22}$	C1 A1	<b>ecf (a)(ii)</b> <b>accept</b> 6.75 or $6.8 \times 10^{22}$ using 10800
b	i	the average displacement/distance travelled of the electrons <u>along the wire</u> per second; (over time/on average) they move slowly in one direction through the metal/Cu lattice (when there is a p.d. across the wire); (because) they collide constantly/in a short distance with the lattice/AW	B1  B1 B1	no mark for quoting formula <b>allow</b> in one second  <b>max 2 marks</b> from 3 marking points
	ii	select $I = nAev$ ( $= 3.0 A$ ) $v = 3.0/8.0 \times 10^{28} \times 1.1 \times 10^{-7} \times 1.6 \times 10^{-19} = 2.1 \times 10^{-3} (m s^{-1})$	C1 C1 A1	1 mark for correct formula 1 mark for correct substitutions into formula 1 mark for correct answer to 2 or more SF
<b>Total question 1</b>			<b>12</b>	

4)

(a)		V is not proportional to I the characteristic/line is a curve/not a straight line	B1 B1	<b>accept</b> statement of Ohm's law for 1 mark <b>not</b> resistance is not constant/AW
(b)	(i)	variable power supply <b>or</b> fixed supply + potential divider ammeter in series with and voltmeter in parallel with lamp	B1 B1	value of power supply <b>not</b> required <b>accept</b> cross or $\Omega$ in circle for lamp symbol <b>penalise</b> each extra component connected (up to two)
	(ii)	vary p.d. (across lamp)/current (in circuit) by changing voltage supply/moving contact on the potential divider take/record set of values of V and I	B1 B1 B1	<b>accept</b> increase voltage in steps of 1 V/AW <b>accept as ecf</b> changing variable resistor in series in circuit QWC mark
(c)		From Fig. 1.1 lamp $I_L = 0.25 A$ for $R = 6/20 = 0.30 A$ so $I_P = 0.55 (A)$	C1 C1 A1	1 mark for each current; 1 mark for $I_R + I_L$ <b>or</b> $R_L = 6/0.25 = 24 \Omega$ ; $R_s$ in // gives $R_{tot} = 10.9$ ; so $I_P = 6.0/10.9 = 0.55 A$
(d)	(i)	straight line through origin and 300,6	B1	
	(ii)	appreciation that p.d.s across both components add to 6 V attempt to find where current is the same in both components $I_S = 0.16$ to $0.17 (A)$ <b>or</b> $165 \pm 5 \times 10^{-3} A$ <b>or</b> $165 \pm 5 mA$	B1 B1 B1	<b>accept</b> answers in terms of lines drawn on fig.1.1 <b>or</b> description of using ruler horizontally on graph and adding squares across graph, etc. <b>ecf (d)(i)</b>
<b>Total</b>			<b>14</b>	

5)

(a)		resistance = p.d./current	B1	<b>accept</b> voltage instead of p.d.; ratio of voltage to current; voltage per (unit) current <b>not</b> $R = V/I$ or p.d. = current x resistance or p.d. per amp or answer in units or voltage over current
(b)	(i)	6 V	B1	
	(ii)	$R = V/I = 6/0.25$ $= 24 \text{ } (\Omega)$	C1 A1	<b>ecf (b)(i)</b> 240 V gives 960 $\Omega$ <b>award</b> 0.024 $\Omega$ 1 mark only (POT error)
(c)	(i)	6 V supply with potential divider 'input' across it and lamp across p.d. 'output' ammeter in series with lamp voltmeter across lamp	B1  B1 B1	<b>accept</b> 0 – 6 V variable supply with lamp across it <b>not</b> variable R in series with supply circuit with no battery present can only score voltmeter mark
	(ii)	non-zero intercept line indicating increasing value of R with current	B1 B1	curve must reach y-axis <b>accept</b> straight line or upward curve
	(iii)	resistivity/resistance of filament wire increases with temperature the temperature of the lamp increases with current/voltage increase more frequent electron-ion/atom collisions/AW increased ion vibrations	B1 B1	<b>accept</b> any two of the four statements <b>accept</b> AW, e.g the lamp heats up because of the current
(d)	(i)	lamps do not light remaining lamps are lit with qualification	B1 B1	<b>ignore</b> reasons unless too contrary qualification could be more dimly or sensible explanation
	(ii)	using resistors in parallel formula to obtain a value of R per unit $R$ per unit = 19.4 $\Omega$ or $R$ total = 774 $\Omega$ $I = 6/19.4$ or $240/774 = 0.31 \text{ A}$	C1 C1 A1	eg takes $R$ of bulb = 10 $\Omega$ giving $R$ per unit = 9.1 $\Omega$ gains first mark only <b>ecf (b)(i)(ii)</b> <b>accept</b> $R$ of resistors = 4000 $\Omega$ ; current in chain = 0.06 A; total current = 0.06 + 0.25 = 0.31 A 0.3 A is SF error so gains 2 marks only apply <b>SF error only once</b> in paper
<b>Total question 1</b>			<b>16</b>	


6)

Question	Expected Answers	Marks	Additional Guidance	
a	i	no current/no light/does not conduct until V is greater than 1.5 V brightness/intensity of LED increases with current/voltage above 1.5 V above 1.8 V current rises almost linearly with increase in p.d./AW the LED does not obey Ohm's law as I is not proportional to V/AW below 1.5 V, LED acts as an infinite R/ very high R/acts as open switch above 1.5 V, LED resistance decreases (with increasing current/voltage)	B1 B1 B1 M1 A1 B1 B1	<b>allow</b> 1.4 to 1.6 V (QWC mark) (alternative QWC mark)  <b>max 5 marks</b> which must include at least one of the first 2 marking points
	ii 1 2	infinite resistance $I = 23.0 \pm 1.0 \text{ (mA)}$ $R = 1.9 \times 10^3 / (23 \pm 1) = 83 \pm 4 \text{ } \Omega$	B1 C1 A1	<b>apply</b> POT error for 0.083 $\Omega$
b	LED symbol with correct orientation resistor (need not be labelled) and ammeter in series with it voltmeter in parallel across LED only	B1 B1 B1	diode symbol + circle + at least one arrow pointing away	
c	the resistor limits the <u>current</u> in the circuit (when the LED conducts) otherwise it could overheat/burn out/be damaged/AW	B1 B1		
d	in fig 4.3 the <u>voltage</u> range is from zero to maximum possible in fig. 4.2 the resistance variation is small/AW (so) in fig. 4.2 voltage variation across LED is small	B1 B1 B1	<b>allow</b> 6.0 V <b>accept</b> the LED is part of a potential divider <b>accept</b> only at the top end of the range/AW	
<b>Total question 4</b>		<b>16</b>		

7)

a	i	When <u>connected/using/AW</u> to the <u>230 V</u> supply  the <u>power/energy per second</u> from supply/output/dissipated/AW is <u>25 W</u>	B1 B1	<b>accept</b> when working normally/AW <b>not</b> 230 V (going) through/into lamp/AW <b>accept</b> transferred from electrical (into other) form(s) is 25 W
	ii	$25 = 230^2/R$ $R = 2100 \Omega$ <b>or</b> 2.1 k $\Omega$	C1 A1	<b>accept</b> $I = 25/230 = 0.11$ A $R = 230/0.11 = 2100 \Omega$ (2116 $\Omega$ )
	iii	Using the equation in the form $P = VI$ , for larger P need larger I so 60 W	M1 A1	accept $P = V^2/R$ , for larger P need smaller R so larger I; do <b>not</b> allow any argument using 880 $\Omega$ unless this value is calculated here
	iv1	$1/R = 1/2100 + 1/880$ $R = 620 \Omega$	C1 A1	substitution into formula for Rs in parallel <b>ecf (a)(ii)</b>
	iv2	$I = 230/620$ $I = 0.37$ (A)	C1 A1	<b>ecf (a)(iv)1</b> using $1/R$ gives 143 kA accept total $P = 85$ W so $I = 85/230 ; = 0.37$ (A)
b		the resistivity/resistance (of a metal) increases with temperature <b>or</b> R is greater when hot(ter) at 6V/low I little heating effect <b>or</b> at 230 V/high I large heating effect	B1 A1	<b>ora</b> less when colder  <b>QWC mark:</b> explanation linked to observations
c	i	(a unit of) <u>energy</u> equal to 3.6 MJ <b>or</b> 1 kW for 1 h/AW	B1	<b>eg</b> 1000 W for 3600 s or similar
	ii	$0.06 \times 8 = 0.48$ (kWh) or $60 \times 8 = 480$ (Wh) $0.48 \times 21 = 10(.1)$ p	C1 A1	no marks for using s instead of h POT error e.g. 100 or 10000 p
<b>Total question 2</b>			<b>15</b>	

8)

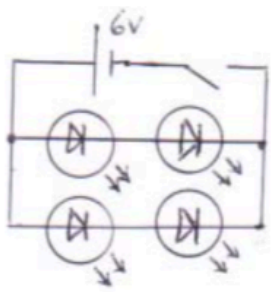a	i	read off value of current (at $V = 6.0$ V)  calculate R using $V/I$	B1 B1	any reference to using gradient scores 0/2 <b>accept</b> $I = 0.25$ (A) or 250 (mA) <b>accept</b> $R = 24 \Omega$
	ii	V is not proportional to I	B1	<b>accept</b> not a straight line; R is not constant
b	i	$Q = It = 0.25 \times 1 = 0.25$ C	B1	<b>ecf(b)(i)</b> <b>ecf b(ii)</b> <b>accept</b> $2.2 \times 10^4$ J; <b>allow</b> 360 J for 1 mark only
	ii	$E = VIt$ or $QV = 6 \times 0.25 = 1.5$ J	B1	
	iii	$E = VIt = 1.5 \times 4 \times 60 \times 60 = 2.16 \times 10^4$ J	C1 A1	
c	i	energy transfer per unit charge from electrical to other forms	B1	<b>or</b> energy transfer/charge; work done /charge <b>or</b> across LED  $3 \times 0.030 = 0.090$ W per LED so $0.090 \times 4$ <b>or</b> 30 mA in two branches at 6 V <b>or</b> total current is 60 mA from 6 V battery
	ii	30 mA	B1	
	iii	Use of $P = VI$ suitable method (may be expressed purely in numerical form) = 0.36 W	A1 M1 A1 A0	
	iv		B1 B1 B1	
d	draws a lower current/ light lasts longer (before battery discharged)/AW <b>or</b> LEDs more efficient (at converting electrical energy into light) <b>or</b> if one LED fails there are still two lit <b>or</b> more robust/longer working life	B1	<b>allow</b> lower power consumption/AW	
<b>Total question 1</b>			<b>16</b>	

9)

(a)	(i)1	infinity	<b>B1</b>	accept symbol
(a)	(i)2	$R = 1.8/10 \times 10^{-3}$ $R = 180 \Omega$	<b>C1</b> <b>A1</b>	0.18 $\Omega$ scores 1 mark
(a)	(ii)	resistance decreases because I increases more than V therefore since $R = V/I$ value decreases/AW	<b>B1</b> <b>B1</b> <b>B1</b>	<b>accept</b> calculation at second value, e.g. at 2.0 $R = 53 \Omega$ , <u>with comparison</u> <b>OR</b> at two other values <b>QWC mark</b> for second marking point
(b)		correct <u>symbol</u> and <u>direction</u> for LED R in series with LED across XY ammeter in series voltmeter in parallel with LED only	<b>B1</b> <b>B1</b> <b>B1</b> <b>B1</b>	circle not essential, internal line optional no variable resistor
(c)		torch; car brake/rear light/ traffic light, etc. torch: draws a lower current / light lasts longer before battery discharged/AW <b>or</b> LEDs (much) more efficient (at converting electrical energy into light)/AW <b>or</b> if one LED fails remainder still lit/AW	<b>M1</b> <b>A1</b>	suitable example <b>accept</b> any <b>one</b> sensible statement, include longer life, more durable contradictory statements score zero
<b>Total</b>			<b>12</b>	

10)

<b>i</b>	V is not proportional to I	<b>B1</b>	<b>accept</b> not a straight line; R is not constant
<b>ii</b>	R (approximately) constant up to $V = 0.5 \text{ V}$ and $I = 50 \text{ mA}$ so $R = 0.5/0.05 = 10 (\Omega)$	<b>B1</b> <b>B1</b>	<b>allow</b> graph is (almost) linear/straight (to $V = 0.5 \text{ V}$ ) or constant gradient <b>allow</b> any correct calculation, e.g. $0.2/0.02$
<b>iii</b>	the resistivity/resistance of the (metal) filament increases with temperature the larger the current in the filament the hotter it becomes/AW	<b>B1</b> <b>B1</b>	<u>larger current</u> heats filament <u>so</u> resistance increases <b>or</b> electron-ion collisions increase/AW; <b>allow</b> atom for ion

11)

<b>a</b>	<b>i</b>	ammeter in series voltmeter in parallel with LED	<b>B1</b>	both correct to score 1 mark
	<b>ii</b>	(at 20 mA) $V_{\text{led}} = 4.0 \text{ V}$ $V_R = 0.020 \times 100 = 2.0 \text{ V}$ so p.d. = 6.0 V	<b>B1</b> <b>C1</b> <b>A1</b>	<b>allow</b> $R_{\text{led}} = (4.0/0.02) = 200 \Omega$ p.d. = $0.020(200 + 100)$ <b>allow</b> answer to 1 SF
<b>b</b>	<b>i</b>	energy in eV = $4.1 \times 10^{-19}/1.6 \times 10^{-19} = 2.6 \text{ (eV)}$	<b>B1</b>	<b>expect</b> 2.56 eV
	<b>ii</b>	LED strikes at 2.6 V/ only conducts above 2.6 V an electron must pass through a p.d. of 2.6 V to lose energy as a photon of blue light/AW.	<b>M1</b> <b>A1</b>	
<b>c</b>	<b>i</b>	$n = I/e = 0.02/1.6 \times 10^{-19}$ $= 1.3 \times 10^{17}$	<b>C1</b> <b>A1</b>	<b>expect</b> $1.25 \times 10^{17}$
	<b>ii</b>	energy/s = $1.25 \times 10^{17} \times 4.1 \times 10^{-19}$ or $2.6 \text{ V} \times 0.020 \text{ A}$ $= 0.051$ to $0.053 \text{ (J s}^{-1}\text{)}$	<b>C1</b> <b>A1</b>	<b>ecf (c)(i); NOT</b> $4.0 \times 0.020$ answer is 0.053 using $1.3 \times 10^{17}$
	<b>iii</b>	efficiency = $0.052/(4.0 \times 20 \times 10^{-3})$ $= 0.64$	<b>C1</b> <b>A1</b>	<b>ecf (c)(ii)</b> <b>accept</b> $V_{\text{strike}}/V_{\text{operate}} = 2.6/4.0$ or any other correct (P or W out)/ (P or W in) calculation <b>accept</b> 64 %
<b>d</b>		shape similar to the curve drawn leaving x-axis at close to 2.0 V and passing through (3.4, 20)	<b>B1</b> <b>B1</b>	Within half a square
<b>Total</b>			<b>15</b>	

<b>d</b>		total current in circuit = $2600/230 = 11.3$ A so 13 A fuse required	M1 A1	<b>accept</b> $I = 2500/230 = 10.9$ A
<b>e</b>	<b>i</b>	(a unit of) <u>energy</u> equal to 3.6 MJ <b>or</b> 1 kW for 1 h/AW	B1	<b>e.g.</b> 1000 W for 3600 s or similar; <b>NOT</b> 1 kW <b>per</b> hour
	<b>ii</b>	$1.6 \times 4 \times 18$ 115 (p)	C1 A1	<b>allow</b> 1 mark for 108 p; i.e. using $1.5 \times 4 \times 18$ <b>or</b> 1 mark for 79 p; i.e. using $1.1 \times 4 \times 18$ <b>NOT</b> 72 p
<b>Total question 1</b>			<b>18</b>	

12)

<b>a</b>	<b>i</b>	straight line through origin passing through (2, 30)	B1 B1	<b>allow</b> $2.0 \pm 0.05$ , i.e. half a square
	<b>ii</b>	V is <u>proportional</u> to I for the resistor R but the LED the characteristic/line is a curve/not a straight line	B1 B1	<b>accept</b> statement of Ohm's law <b>allow</b> $V \propto I$ <b>NOT</b> gradient changes <b>nor</b> gradient not constant
<b>b</b>	<b>i</b>	From Fig. 2.1, V <u>across</u> R at 30 mA = 2.0 V <b>or</b> $0.03 \times 67 = 2.0$ V V <u>across</u> LED = $5.0 - 2.0 = 3.0$ V I in LED at 3.0 V is 30 mA	B1 B1 B1	<b>allow</b> 1 SF answers in <b>b(i)</b> and <b>(ii)</b> at 30 mA R of LED = $100 \Omega$ total R = $167 \Omega$ I in LED = $5.0/167 = 30$ mA <b>or</b> in reverse
	<b>ii 1</b>	0.030 (C)	A1	<b>allow</b> 30 mC or $3.0 \times 10^{-2}$ C
	<b>ii 2</b>	QV or VI = $3.0 \times 0.03$ <b>or</b> $I^2R = 0.03^2 \times 100$ energy = 0.090 (J)	C1 A1	<b>possible ecf from (ii)1</b> <b>allow</b> 90 mJ or $9.0 \times 10^{-2}$ J <b>allow</b> 1 mark for 0.15 (J), i.e. taking $V = 5$ V
	<b>ii 3</b>	$P = I^2R = 0.03^2 \times 67$ = 0.060 (J)	C1 A1	<b>possible ecf from b(i) for R value</b> <b>allow</b> $P = VI = 2.0 \times 0.03 = 0.060$ J <b>or</b> $P = V^2/R = 2.0^2/67 = 0.0597$ J
	<b>iii</b>	current required is 0.63 A so nearest larger value is best 1.0 A	M1 A1	
<b>c</b>		suitable example, e.g. torch bulb, traffic light, car rear lamp, etc. (replaced by cluster of LEDs) advantage, e.g. draws a lower current/ more efficient (at converting electrical energy into light)/if one LED fails others are still lit/greater lifetime/more robust	B1 B1	<b>accept</b> TV screens etc. <b>allow</b> size e.g. back lighting in mobile <b>NOT</b> cost
<b>Total question 2</b>			<b>16</b>	